
Power Supplies & Regulators

Exercise Book

IESE Exercise Book 3 of 3

Problems only — attempt them first; answers (final results, no worked steps) are at the back.

How to use this book

This is the problem set distilled from the *Power Supplies & Regulators* solving manual. It contains **only exercises and their answers** — no theory and no worked derivations. Each chapter mirrors a chapter of the manual, so when you are stuck on a *method*, open the manual at the same chapter and read its Protocol and Worked Example.

Key Idea

Sizing exercises run *backwards*, from the load to the wall: fix the regulator's headroom first, then the ripple, then the diode drops, then the worst-case mains. The answer key gives the standard part/value reached at the end — get there yourself before you look.

Contents

How to use this book	ii
1 Specifications: reading the data sheet	1
2 The classical (transformer) power supply	2
3 Power factor and its correction	3
4 Linear voltage regulators	4
5 Switching regulators	5
6 Laboratory: Buck converter	6
7 Answers	7

Chapter 1

Specifications: reading the data sheet

Exercise 1.1 A datasheet line by line

A 5 V regulator's table reads: $\Delta V_{out} = 10 \text{ mV}$ for I_{out} from 5 mA to 1.5 A; $\Delta V_{out} = 3 \text{ mV}$ for V_{in} from 8 V to 12 V. (a) Load and line sensitivity, and the ripple rejection in dB. (b) At $V_{in} = 12 \text{ V}$, $I_{out} = 1 \text{ A}$: efficiency and dissipated power.

Exercise 1.2 Reading the numbers

A regulator shows $\Delta V_{out} = 7 \text{ mV}$ over an input range $\Delta V_{in} = 17.5 \text{ V}$, and $\Delta V_{out} = 30 \text{ mV}$ for a load step $\Delta I_{out} = 1.5 \text{ A}$. Find the ripple rejection (dB) and the output resistance.

Chapter 2

The classical (transformer) power supply

Exercise 2.1 Size the secondary

Size the supply for 12 V/0.5 A from a 7812 ($V_{DO,min} = 2\text{ V}$), full-wave bridge with $V_D = 1\text{ V}$, ripple $\Delta V \leq 1\text{ V}$, mains $230 \pm 10\%$ at 50 Hz. (a) The filter capacitor. (b) The secondary RMS voltage and the turns ratio. (c) Why would a *half-wave* rectifier double the capacitor?

Exercise 2.2 Filter capacitor

Full-wave, $f = 50\text{ Hz}$, $V_{MAX} = 9\text{ V}$, $I_{out} = 100\text{ mA}$, $C = 2.2\text{ mF}$ (use $T_{dis} = T$). Find the ripple ΔV , the conduction time t_c and the peak charging current I_{peak} .

Exercise 2.3 The capacitor trade-off

Repeat the previous exercise with $C' = 4.7\text{ mF}$ (same f, V_{MAX}, I_{out}). What happens to ΔV and to I_{peak} ?

Chapter 3

Power factor and its correction

Exercise 3.1 R - L load and its correction

$R = 3\ \Omega$, $L = 10.6\ \text{mH}$, $V_S = 480\ \text{V}_{\text{RMS}}$ at $f = 60\ \text{Hz}$ ($\omega = 377\ \text{rad/s}$). (a) Find $|I_S|$, φ , S , P and the power factor. (b) Find the parallel capacitor that corrects PF to 1, and the new source current.

Exercise 3.2 The pure inductor

A purely inductive load $L = 10.6\ \text{mH}$ (no R), same source as above. (a) Find $|I_S|$ and the power factor. (b) Find the parallel C that brings the source current to zero.

Chapter 4

Linear voltage regulators

Exercise 4.1 7805 at light load

A 7805 supplies $I_{out} = 200\text{ mA}$ from $V_{in} = 8\text{ V}$. (a) Dissipation, efficiency, and is the bare package ($R_{th} = 60\text{ K/W}$) enough at $T_{amb} = 25^\circ\text{C}$? (b) What is the lowest rippled-input *valley* that still regulates?

Exercise 4.2 7805 needs a heat sink

A 7805 supplies $I_{out} = 1\text{ A}$ from $V_{in} = 12\text{ V}$. Find the dissipation and efficiency, and the junction temperature rise both bare (60 K/W) and with a 10 K/W heat sink.

Exercise 4.3 Efficiency ceiling

For a 78xx ($V_{DO,min} = 2\text{ V}$), give the maximum efficiency $\eta_{MAX} = V_{out}/(V_{out} + 2)$ for $V_{out} = 3.3\text{ V}$, 5 V and 12 V .

Chapter 5

Switching regulators

Exercise 5.1 Buck duty cycle

A buck converter makes $V_{out} = 5\text{ V}$ from $V_{in} = (9 \pm 1)\text{ V}$. Give the nominal duty cycle δ and its range over the input range.

Exercise 5.2 Boost from a battery

A 12 V rail must come from a battery $V_{in} = (5 \pm 0.5)\text{ V}$, $f_{SW} = 200\text{ kHz}$. (a) Topology and the δ range. (b) With a capacitor-current swing $\Delta I_C = 1.2\text{ A}$ and $\text{ESR} = 50\text{ m}\Omega$, the output ripple. (c) Why is this topology's feedback loop deliberately made *slow*?

Exercise 5.3 Minimum L for CCM

A buck has $V_{in} = 9\text{ V}$, $V_{out} = 5\text{ V}$ ($\delta = 0.556$), $f_{SW} = 100\text{ kHz}$, lightest load $I_{out,min} = 50\text{ mA}$. Find the smallest L that keeps it in CCM and give the next standard value.

Chapter 6

Laboratory: Buck converter

Exercise 6.1 CCM or DCM?

For a buck with the boundary (critical) current $I_B = \frac{V_{out}(V_{in} - V_{out})}{2Lf_{sw}V_{in}}$, decide the conduction mode: (a) $V_{in} = 8\text{ V}$, $V_{out} = 5\text{ V}$, $R_L = 30.5\ \Omega$, $I_B \approx 0.11\text{ A}$; (b) $V_{in} = 24\text{ V}$, $V_{out} = 5\text{ V}$, $R_L = 50\ \Omega$, $I_B \approx 0.23\text{ A}$.

Chapter 7

Answers

Final results only — the matching chapter of the *manual* shows how each is obtained.

Chapter 1 — Specifications

1.1 (a) $S_I = 0.010/1.495 \approx 6.7 \text{ m}\Omega$; $S_V = 0.003/4 = 0.75 \text{ mV/V}$; ripple rejection $= 20 \log_{10}(4/0.003) = 62.5 \text{ dB}$. (b) $P_{out} = 5 \text{ W}$, $P_{in} \approx 12 \text{ W}$: $\eta = 41.7\%$, $P_d = 7 \text{ W}$ of heat.

1.2 Ripple rejection $= 20 \log_{10}(17.5/0.007) = 68 \text{ dB}$; $S_I = 0.030/1.5 = 20 \text{ m}\Omega$.

Chapter 2 — The classical (transformer) power supply

2.1 (a) $C = I_{out}(T/2)/\Delta V = 5 \text{ mF}$. (b) $V_{MAX} = 15 \text{ V}$, secondary peak 17 V , $V_{S,RMS} = 12.0 \text{ V}$; at -10% that is $13.4 \text{ V} \Rightarrow$ pick a 15 V_{RMS} secondary, ratio $\approx 230/15 = 15.3$. (c) Half-wave discharges for the whole period T , twice as long, so the same ΔV needs $C = 10 \text{ mF}$.

2.2 $\Delta V = 0.9 \text{ V}$, $t_c = 1.44 \text{ ms}$, $I_{peak} = 2.77 \text{ A}$.

2.3 $\Delta V' = 0.43 \text{ V}$ (smaller), $t'_c = 0.98 \text{ ms}$, $I'_{peak} = 4.1 \text{ A}$ (larger) — lower ripple, higher current peak.

Chapter 3 — Power factor and its correction

3.1 (a) $\omega L = 4 \Omega$, $|Z| = 5 \Omega$, $|I_S| = 96 \text{ A}$, $\varphi = 53.1^\circ$, $S = 46.08 \text{ kVA}$, $P = 27.67 \text{ kW}$, $PF = 0.6$. (b) $C = L/(\omega^2 L^2 + R^2) = 424.5 \mu\text{F}$; source current drops to 58 A , $PF = 1$.

3.2 (a) $|I_S| = V_S/(\omega L) = 120 \text{ A}$, $\varphi = 90^\circ$, $PF = 0$. (b) $C = 1/(\omega^2 L) = 663.8 \mu\text{F}$ (resonance), ideally $I_S = 0$.

Chapter 4 — Linear voltage regulators

4.1 (a) $P_{reg} = 0.6 \text{ W}$, $\eta = 62.5\%$; junction rise $36 \text{ K} \Rightarrow T_j \approx 61^\circ\text{C}$ — fine without a heat sink. (b) $V_{MIN} = V_{out} + V_{DO,min} = 7 \text{ V}$.

4.2 $P_{reg} = 7 \text{ W}$, $\eta = 42\%$; bare rise 420 K (far past the 125°C limit), with 10 K/W rise $70 \text{ K} \Rightarrow T_j \approx 95^\circ\text{C}$ (acceptable).

4.3 $\eta_{MAX} = 62.3\%$ (3.3 V), 71.4% (5 V), 85.7% (12 V).

Chapter 5 — Switching regulators

5.1 $\delta = V_{out}/V_{in} = 55.5\%$; range 50% ($V_{in} = 10\text{ V}$) to 62.5% ($V_{in} = 8\text{ V}$).

5.2 (a) $V_{out} > V_{in}$: **Boost**, $\delta = 1 - V_{in}/V_{out}$, range $62.5\% \dots 54.2\%$ (nominal 58.3%).
(b) $\Delta V_{out} = \Delta I_C \cdot \text{ESR} = 60\text{ mV}$. (c) The boost is prone to instability, so its loop is given a low bandwidth — it reacts slowly but will not oscillate.

5.3 $L_{min} = \frac{(V_{in} - V_{out})\delta}{2I_{out,min}f_{SW}} = 222\text{ }\mu\text{H}$; pick the next standard $330\text{ }\mu\text{H}$ ($\Delta I_L \approx 67\text{ mA}$, CCM holds).

Chapter 6 — Laboratory: Buck converter

6.1 (a) $I_{out} = V_{out}/R_L \approx 0.16\text{ A} > I_B \Rightarrow \text{CCM}$. (b) $I_{out} \approx 0.10\text{ A} < I_B \Rightarrow \text{DCM}$ (light load at a high step-down ratio).